



THE COUNCIL OF COMMUNITY COLLEGES OF JAMAICA

ASSOCIATE OF SCIENCE EXAMINATION

SEMESTER I – 2014 DECEMBER

PROGRAMMES: COMPUTER SERVICING AND ELECTRONICS

COURSE NAME: FUNDAMENTALS OF ELECTRONICS
CODE : (ELEC1103)

YEAR GROUP: ONE

DATE: MONDAY, 2014 DECEMBER 15

TIME: 1:00 P.M. – 4:00 P.M.

DURATION: 3 HOURS

EXAMINATION TYPE: FINAL

This Examination paper has 6 pages

INSTRUCTIONS:


SECTION B: ANSWER ANY THREE (3) QUESTIONS FROM THIS SECTION.

SECTION B


*Instructions: Answer any **THREE (3)** questions from this section.*

Question 1

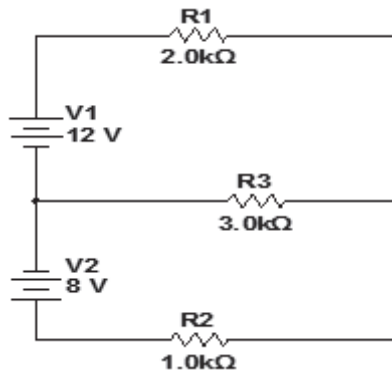
- a. Name and state Kirchhoff's **two (2)** laws. (2 marks)
- b. Using the laws stated in part (b) above, solve for the values of I_1 , I_2 & I_3 in the circuit below. (8 marks)



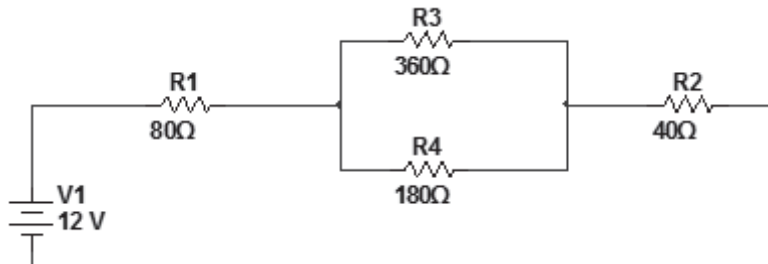- c. In the circuit below solve for the effective resistance and the current leaving the source. (5 marks)



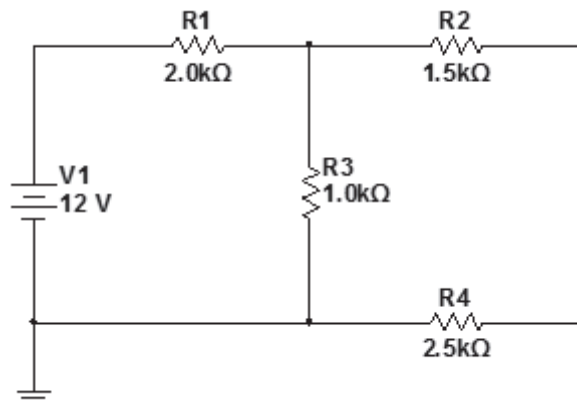- d. By applying the principle of mesh analysis to the circuit shown below



i. Determine the value of each mesh current. (8 marks)

ii. The current following through R_3 . (2 marks)

(Total 25 marks)

Question 2


a. State and explain **two (2)** factors that affect the induce e.m.f of an inductor. (4 marks)

b. State Faraday's laws. (2 marks)

c. With the aid of a diagram **BRIEFLY** explain Fleming's right hand rule. (4 marks)

d. Solve for effective inductance, if two (2) identical solenoid inductors each containing 200 turns, with length 0.05m and cross-sectional area $8 \times 10^{-5} \text{m}^2$ are connected in series. (4 marks)

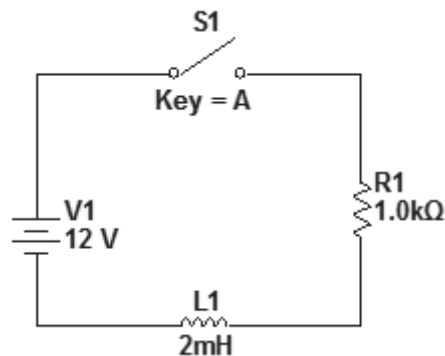e. The circuit below consists of an inductor and a resistor in series with a power source. Use the principle of circuit analysis and any other method to complete the following:



i. The current in circuit just after the switch is closed. (1 mark)

ii. The current in circuit after a long period (t). (2 marks)

iii. The energy stored by the inductor. (3 marks)


iv. The inductor's time constant. (2 marks)

v. The voltage across resistor at $t =$ time constant. (3 marks)

(Total 25 marks)


Question 3

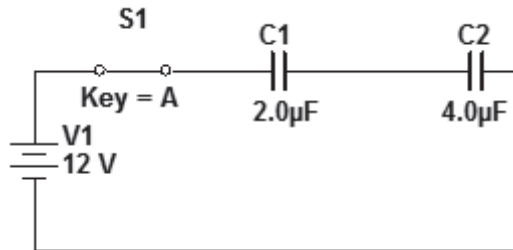- a. Define the farad. *(2 marks)*
- b. Two capacitors C_1 and C_2 are used to construct the circuit as shown below.



Assuming that the switch has been close for a long time solve for the following:

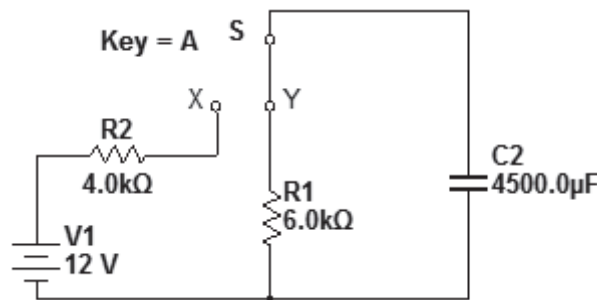- i. The effective capacitance of the circuit. *(3 marks)*
 - ii. The total charge acquired by capacitor C_2 . *(2 marks)*
 - iii. The voltage across capacitor C_1 . *(2 marks)*
- c. A typical air capacitor is designed using plates of area 100.0 cm^2 and a separation 1.0 cm . If the capacitor is then connected to 9 V battery, determine:
- i. The capacitance of the capacitor. *(3 marks)*
 - ii. The amount of charge stored on each plate. *(2 marks)*
 - iii. The electric field across the plates of the capacitor. *(2 marks)*
 - iv. The energy stored by the capacitor. *(2 marks)*
- d. A DC CR network is designed using a single resistor and capacitor as shown in the circuit below.




- i. At what position must the switch be for the capacitor to be charged? *(1 mark)*

- ii. Solve for the time constant when the capacitor is being charged and complete the equation for the charging process. *(2 marks)*
- iii. In the discharging process how long does it take for the capacitor to reach 25% of its energy stored? *(4 marks)*

(Total 25 marks)

Question 4

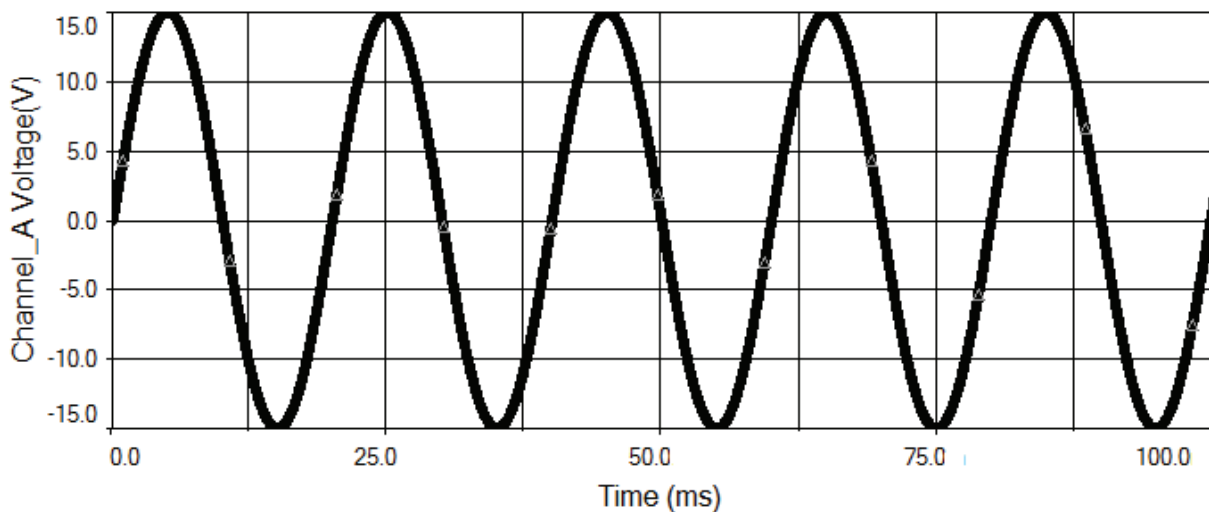- a. Differentiate between:
 - i. Magnetism and electromagnetism. *(2 marks)*
 - ii. Relative and absolute permeability. *(2 marks)*
- b. Calculate the magnetic flux density for each of the devices given below:
 - i. 5cm from a long straight wire carrying a current of 10 A. *(3 marks)*
 - ii. A long solenoid of 500 turns and length 10cm carrying 5A. *(3 marks)*
- c. An AC source was analyzed by a group of students on a CRO and a snapshot of the wave form was obtained.



From the wave form given in the diagram above complete the following:

- i. The period of the AC source in seconds. *(2 marks)*
- ii. The frequency of the wave. *(2 marks)*

- iii. The peak to peak value of the wave. *(2 marks)*
- iv. The wave's angular frequency. *(3 marks)*
- v. Derive an expression (equation) for the wave shown. *(3 marks)*
- vi. Determine the value of the voltage at $t = 3\text{ms}$. *(3 marks)*

(Total 25 marks)

Question 5

- a. In an AC circuit, what is meant by the term impedance? *(2 marks)*
- b. Distinguish between inductive reactance and capacitive reactance. *(3 marks)*
- c. Explain briefly the behaviour between the voltage and the current for both RC and RL circuits. *(4 marks)*
- d. In analyzing the behaviour of series RLC circuit a student was provided with a 12V AC 50Hz power supply, a 40 resistor, a 0.16H inductor and a $1.6 \times 10^{-4}\text{F}$ capacitor. Using the information given complete the following:
 - i. Draw a diagram outlining the circuit to be designed. *(3 marks)*
 - ii. Solve for the inductive reactance (X_L). *(3 marks)*
 - iii. Solve for the capacitive reactance (X_C). *(3 marks)*
 - iv. Calculate the impedance of the circuit. *(4 marks)*
 - v. Determine the current that will flow in the circuit. *(3 marks)*

(Total 25 marks)

END OF EXAMINATION