



THE COUNCIL OF COMMUNITY COLLEGES OF JAMAICA
ASSOCIATE OF SCIENCE EXAMINATION

SEMESTER II – 2019 MAY

PROGRAMME: ENGINEERING

COURSE NAME: INTRODUCTION TO ELECTRONIC DEVICES AND CIRCUITS

CODE: ELEC2409

YEAR GROUP: TWO

DATE: WEDNESDAY, 2019 MAY 8

TIME: 9:00 A.M. – 11:00 A.M.

DURATION: 2 HOURS

EXAMINATION TYPE: FINAL

This Examination Paper has 6 Pages

INSTRUCTION:


- 1. THIS PAPER CONSISTS OF SIX (6) QUESTIONS. ANSWER ANY FOUR (4)**

DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO

Instruction: In the booklet provided, answer any **FOUR (4)** questions.

Question 1

 - A. Sketch the biasing diagrams and circuit symbols for the NPN and PNP transistors with a Common Base Configuration. (6 marks)
- B. For the emitter-stabilized bias circuit below, $V_{CC} = 20V$, $R_B = 510k\Omega$, $R_C = 2.4k\Omega$ and $R_E = 1.5k\Omega$ with $\beta = 100$.



Determine:


- i. I_{Bq}
- ii. I_{Cq}
- iii. V_{CEq}
- iv. V_C
- v. V_E
- vi. V_B
- vii. V_{BC}

(14 marks)


(Total 20 marks)

Question 2

 - A. State the name of the re-joins X, Y & Z in the figure below. (3 marks)
- B. Briefly explain the design properties for biasing a transistor at the following Q points (A, B, C, D) in the figure below. (8 marks)



 - C. Describe the conditions that will result in the following Q point variations below.



(9 marks)

(Total 20 marks)


Question 3

- A. Explain the difference between Intrinsic and Extrinsic semiconductor materials. (4 marks)
- B. i. What are the majority carriers of an **n-Type** and **p-Type** semiconductors? (1 mark)
 ii. List **TWO (2)** elements that constitute the doping process of an **n-Type** semiconductor material. (1 mark)
- C. Sketch the covalent bonding of silicon atoms with the antimony impurity atom. (4 marks)
- D. Describe with the aid of relevant diagrams for a Junction Diode the terms:
 i. *forward bias*
 ii. *reverse bias* (10 marks)

(Total 20 marks)

QUESTION 5

 
- A. Sketch the piecewise-linear equivalent circuit for a typical silicon diode. (5 marks)
- B. State the **THREE (3)** types of Transistor Configurations. (3 marks)
- C. For the circuit shown in the figure below, calculate the:
 i. DC bias voltage V_{CE}
 ii. base current I_B
 iii. collector current I_C (12 marks)



(Total 20 marks)


Question 4

 A. Draw the output waveform, V_o , for the clamping network for the square wave with a max. input of 60 V.



(6 marks)

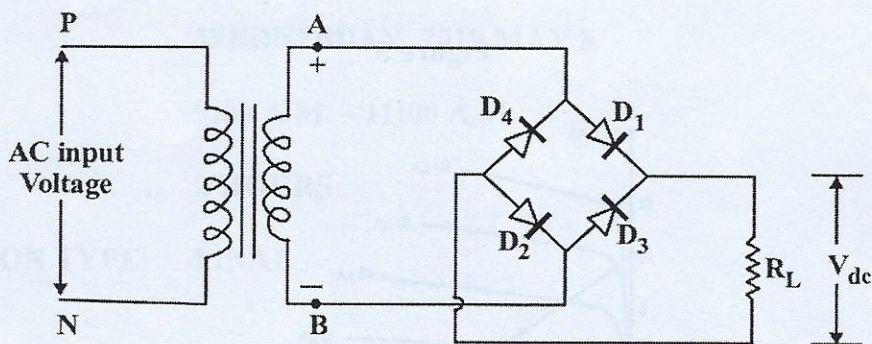B. The full-wave bridge rectifier circuit shown above is supplied with 118.43 peak sinusoidal input voltage and a load resistor of $1K\Omega$



- i. Draw the wave form that the load resistor would see. (2 marks)
- ii. Assuming diodes are ideal, what is the dc voltage available at the load resistor? (4 marks)
- iii. If silicon diodes are employed, what is the dc voltage available at the load? (3 marks)
- iv. Determine the required PIV rating for each Si diode. (2 marks)
- v. Find the max current through each diode during conduction. (3 marks)

(Total 20 marks)

Question 6

- A. Explain the terms **N-Channel** and **P-Channel** field effect transistors. (4 marks)
- B. Use a diagram to explain the construction of an **N-Channel** field effect transistor. (8 marks)
- C. Given the load line of Figure below and the defined Q-point, determine the required values of V_{CC} , R_C and R_B for the fixed-bias configuration.

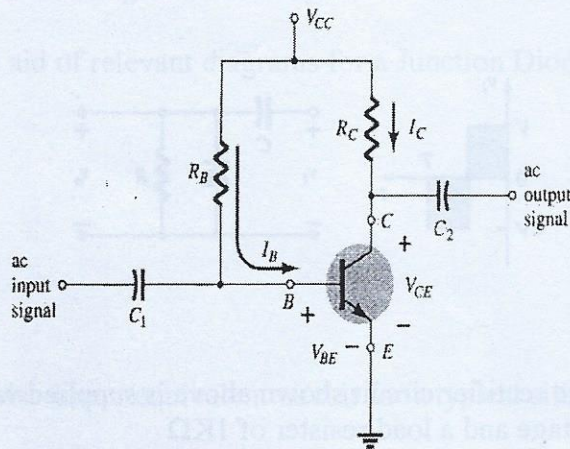


Figure 5

 


Figure 6

(8 marks)

(Total 20 marks)

END OF EXAMINATION